

EED 359 - Digital System Design with FPGA's


Assignment-2

Spring 2017

- a) Write Verilog code to design ALU with following Operations

Operations: Addition, Subtraction, Multiplication and Arithmetic Shifts (Left and Right)
Synthesize the same with Xilinx Nexys4 FPGA target. Also simulate the same using iSim software.

 - b) Write a Verilog code to design and implement the following Combinational Circuit to drive LEDs. On NEXYS4 FPGA board



- c) Write a Verilog code to design and implement 4-bit shift register. First simulate the design in Vivado ISIM and then synthesize the same on Nexys4 FPGA

- d) Write a Verilog code to design and implement BCD counter (00-99) with delay approx. 1sec for each count. Run the design on the FPGA to observe the outputs on LCD